

# leXsolar-PV Professional

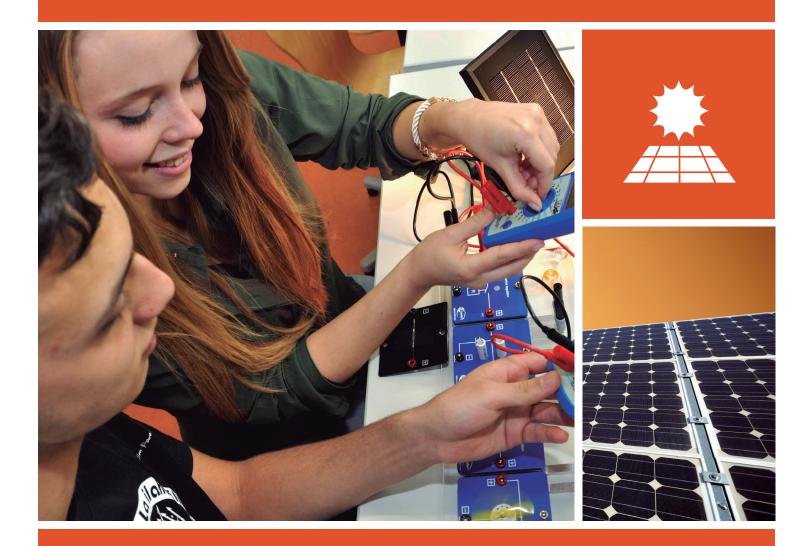

# Instructions manual

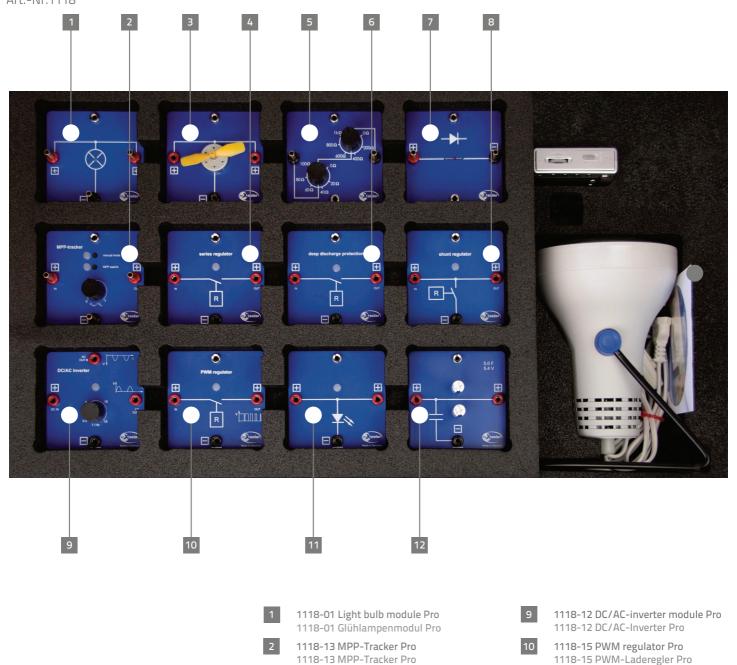

Layout diagram leXsolar-PV Professional Item-No.1118 Bestückungsplan leXsolar-PV Professional Art.-Nr.1118



1x 1118-02 Motor module Pro with

1118-10 Series regulator module Pro

1118-04 Potentiometer module Pro

1118-06 Shunt regulator module Pro

1118-06 Shunt-Regler-Modul Pro

1118-07 Deep discharge protection module Pro 1118-07 Tiefentladeschutzmodul Pro

1118-04 Potentiometermodul Pro

1118-02 Motormodul Pro mit

L2-02-017 Propeller

L2-02-017 Propeller

1118-10 Serienregler Pro

1118-05 Diode module Pro

1118-05 Diodenmodul Pro

11

12

3

4

5

6

8

L3-03-181\_07.06.2017

( RoHS2

1118-08 LED module high brightness Pro

1118-08 LED-Modul superhell Pro

1118-11 Capacitor module Pro 1118-11 Kondensatormodul Pro



Layout diagram leXsolar-PV Professional Item-No.1118 Bestückungsplan leXsolar-PV Professional Art.-Nr.1118



CE RoHS2

3xL2-05-068 Safety short-circuit plug 3xL2-05-068 Sicherheits-Kurzschlussstecker

# **IeXsolar-PV Professional**

## Instructions manual

1. General Information	
1.1 Components	
1.2 Handling and safety	8
2. Electrical basic experiments	9
B.1 Setup of a simple circuit	9
B.2 Ohm`s law	
B.3 Series connection of ohmic resistances	
B.4 Parallel connection of ohmic resistances	
B.5 Start-up and idling behavior of a motor	
3. Basic photovoltaic experiments	
3.0 What is photovoltaics?	
3.1 Series and parallel connection of solar cells (phenomenologic	cal)17
3.2 Series and parallel connection of solar cells (quantitative)	
3.3 Dependence of the power of the solar cell on its area	
3.4 Dependence of the solar cell power on the angle of incident	of the light23
3.5 Dependence of the solar cell power on the illumination inten	sity25
3.6 Dependence of the on-load power on the illumination intens	ity27
3.7 Dependence of the internal resistance on the illumination in	ensity29
3.8. Partial shading of series-connected solar cells	
3.9 Dependence of the power of the solar cell on the temperature	re33
4. I-V-characteristics of a solar cell	
4.1 I-V-characteristics under dark conditions	
4.2 I-V-characteristics, MPP and filling factor of the solar cell	
4.3 Dependence of the I-V-characteristics on the illumination int	ensity39
4.4 Dependence of the I-V-characteristics of the solar cell on the	temperature41
4.5 I-V-characteristics of different solar modules	
4.6 I-V-characteristics of partial shaded solar modules	


5. Components of a solar off-grid system	
6. Possible operating conditions of an off-grid system	51
7. Mode of operation of a shunt regulator and a series regulator	53
8. Experiments with PWM-regulator	
8.1 Comparison of a PWM-regulator and a series regulator	56
8.2 The charge characteristics of a PWM-regulator	58
9. Experiments with MPP-tracker	59
9.1 Working principle of the MPP-tracker module	59
9.2 Characteristics of the MPP-tracker	61
9.3 Comparison of shunt regulator and MPP-tracker for the capacitor charge curve	64
10. Mode of operation of the deep discharge protection module	
11. Experiments with DC/AC inverter	69
11.1 Working principle of a DC/AC inverter module	69
11.2 Determination of the output voltage course at the DC/AC inverter	70

## 1. General Information

## **1.1 Components**

The following part contains information about the components of the experimental system. There is sketched a photograph and a small pictogram how the modules are displayed in the experimental setup. Furthermore you get information about the handling of the components.

#### Base unit

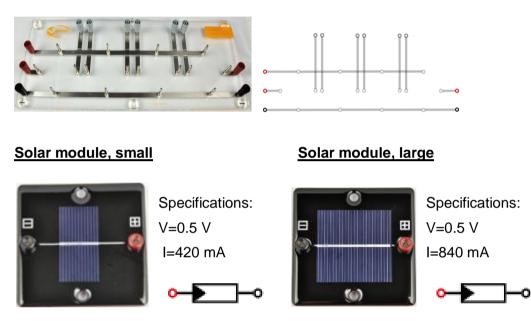

#### Solar module, extra large



### Diode module













#### Resistor plug module (triple) with resistor plug elements



The following resistor plug elements are included:

2 x R=10Ω 1 x R=33Ω 3 x R=100Ω



#### Light bulb module



The light bulb module starts lighting at a voltage of about 0.5V. However, the light bulb is more glowing, than lighting very bright. For an optimum visibility the light bulb should be shaded from other light sources.

#### LED module



The LED module corresponds to a LED lamp in a real solar off-grid system. For efficiency reasons nearly exclusively LEDs are used in such systems.

#### Motor module



Starting current I=20mA

Starting voltage V= 0.4V

Running voltage V=0.4V...12V





#### Capacitor module



Specifications: Double module: V=5.4 V C=5.0F

Single module: Internal resistance R < 34mΩ Max. current I=10A



#### Deep discharge protection



A deep discharge protection is a device that protects an accumulator from dropping below the minimum charging voltage. Deep discharge is harmful for many types of accumulators; especially for lead accumulators, that are often used in off-grid systems; and leads to a drastic increase of their lifetime. In real systems the deep discharge protection is integrated in the charge control, but in this experimental system both devices are divided due to didactic reasons. The leXsolar deep discharge protection is a so called two-level controller that disconnects the consumer from the accumulator when the loading voltage is dropping below 2.8V. Only when the accumulator is

charged again up to 3.16V, the consumer is switched on. The control LED is lighting, as long as the consumer is switched on.

#### Shunt-regulator



The shunt-regulator is a charge controller that short circuits the input voltage when reaching the charge end voltage to protect the accumulator from overload. It is a two-level controller with an upper switching threshold of 4.2V and a lower switching threshold of 3.6V. The working principle of the control LED is identical to the series regulator. Before starting the experiment, the capacitor should be loaded up to 2V to ensure the correct operation of the control LED.

#### PWM-regulator



So called pulse width modulators do not load the accumulators continuously but with pulses of fixed frequency and different length. The ratio of pulse duration and pulse period – the so called duty cycle – determines how fast the accumulator is loaded. With this process one can ensure that the accumulator is kept on its maximum capacity as long as no consumer is connected. The advantage over the

two-level regulators is that the loading voltage is not dropping to the lower switching threshold. The leXsolar PWM-regulator has two operating modes: Until a loading voltage of 3.7V the PWM regulator fully interconnects the input voltage. Accordingly it begins to pulse

and reduces the duty voltage until a constant loading voltage of 4.1V is adjusted. The control LED is lighting as long as the PWM-regulator is loading.

#### Series regulator



The leXsolar series regulator is a two-level regulator that disconnects the accumulator from the solar module when the charging voltage of 4.1V is reached. When discharging the accumulator the series regulator interconnects the input voltage of the solar module not before dropping below the lower threshold of 3.5V. The control LED is lighting as long as the series regulator is loading.



鼤

o



#### DC/AC inverter module



DC/AC inverters are used to convert the DC voltage of the solar module into an AC voltage to either feed the electricity into the grid or to operate customary domestic appliances in a smart-grid system. The leXsolar DC/AC inverter module does not produce mains voltage but an AC voltage with an amplitude of 2.5V and a variable frequency that can be adjusted with the potentiometer between 0.5

and 15 Hz. To reduce the power dissipation the process of inverting the voltage has been kept on a simple level. Therefore the output voltage is sinusoidal only in a first approximation.

MPP - Tracker



When connecting an arbitrary consumer to the solar module, it will commonly not operate at the MPP (<u>Maximum Power Point</u>) of the module. Therefore, often a part of the solar cell power is lost because of not using the possible maximum power. An MPP-Tracker is a so called DC/DC inverter which can increase or decrease the input voltage. The power as the product of voltage and current remains constant but the operating point can be adapted to a more convenient part of the I-V-characteristic. The leXsolar MPP-Tracker module has

two operation modes that can be chosen with pushbuttons. When choosing the "automatic mode" the output voltage is varied in a broad range (LED is blinking) and the operating point with the

maximum output power is automatically selected (LED shines continuously). Afterwards, the operating point is slightly shifted, to ensure that the consumer always extracts the maximum power from the solar module (dissipation power is disregarded). When using the "manual mode", the ratio between output and input voltage can be adjusted manually with the potentiometer and a manual tracking is possible. To reduce the power dissipation of the MPP-Tracker module, it is only possible to reduce the output voltage against the input voltage. This is an advantage when the consumer has a lower internal resistance than the solar module.

#### PowerModule



The PowerModule is a compact and intuitively usable voltage source. First, the attached power adapter has to be connected to a power outlet and to the top right input jack. The voltage can be chosen with the "+"- and "-" -buttons and will be displayed by LEDs. When the desired voltage is chosen, the voltage will be applied by using the yellow on/off- button. In case of a short circuit or currents greater than 2 A the PowerModule will switch off immediately.



Specifications:

- Output voltage: 0-12 V
- Output power: max. 24 W
- Adjustable in 0.5 V steps
- Overcurrent detection >2 A and automatic shutoff

Input voltage: 110-230 V, 50-60 Hz (with enclosed power adapter)



#### AV-Module



The AV-Module is a combined voltage and current meter. It holds 3 buttons, whose features are described in the display respectively. By pushing a random button the module will switch on. In the disabled state the display shows the leXsolar emblem. When the display does not show anything or the word "Bat" is shown, it is necessary to change the batteries in the back (2 x AA batteries 1.2 to 1.5V; Take care of the polarity marked on the bottom of the battery case! Do not touch the button while inserting the batteries).



With the top right button the measuring mode can be switched between voltage mode, current mode or combined voltage-current mode. Both measurement mode and required cable connection will be indicated by the circuit symbols on the display. Take care that in voltage mode no current is

applied to the right jack. In the combined mode the voltage can be measured

with the right jack as well as with the left one. The influence of the internal resistance of the current measurement is compensated internally. The measured values are signed. When the positive pole is connected to a red jack and the negative pole is connected to the black jack, the value of the voltage will be positive. When current is applied from the left to the right, the current value will be positive, as well. The other way around, the algebraic sign changes.

After 30 min without pushing a button or after 10 min of measuring a constant value, the module will switch off automatically. It can measure voltages up to 12 V and currents up to 2 A. In case of exceeding one of the values, the module interrupts the current flow and shows "overcurrent" or "overvoltage". This error message can be confirmed by touching a button. The module will resumes measuring, when the values attain acceptable values.

Specifications:

Voltage metering:

- range: 0...12 V
- accuracy: 1 mV
- automatic shutoff in case of overvoltage >12 V
- Current metering:
- range: 0...2 A
- accuracy: 0.1 mA (0...199 mA) und 1mA (200 mA...1 A)
- automatic shutoff in case of overcurrent >2 A
- internal resistance <0.5 Ohm (0...200 mA); <0.2 Ohm (200 mA...2 A)



### 1.2 Handling and safety

## Solar module with stand



The solar module is adjusted against the lamp and stabilized with the stand. The minimum distance between the lamp and the solar module should be **25cm**.



The angle of incidence can be varied by means of the stand. The following angles can be adjusted (printed on the stand):

0°,15°,30°,45° und 55°.

The short circuit current of the solar module can be adjusted by the variation of the angle or the distance between lamp and solar module.



The lamp may become very hot during operation! After using it, the lamp should cool down and not be put back into the case before it is cold enough. Otherwise the foam insert could be damaged.


## 2. Electrical basic experiments

## Experiment B.1

## **B.1 Setup of a simple circuit**

#### Task

Set up a simple electrical circuit.

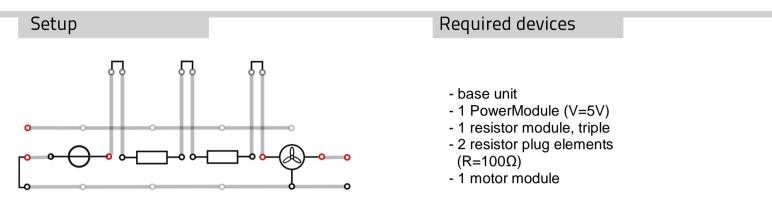


#### Execution

- 1. Set up the experiment according to the circuit diagram. Plug in every resistor module one resistor.
- 2. Open and close the electrical circuit by:
  - a) Plug in/plug off a cable.
  - b) Plug in/plug off a current bridge.
  - c) Plug in/plug off a resistor
- 3. Note your observations.

## Observation

### Evaluation

 1. Formulate reasons for the behaviour of the motor.




## **B.2 Ohm`s law**

## Task

Investigate Ohm's law with several resistors.

## Setup

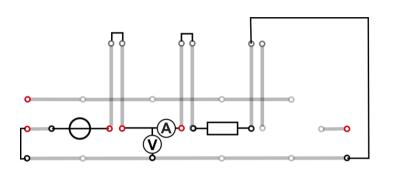

## **Required devices**

- base unit
- 1 PowerModule
- 1 resistor module, triple
- 3 resistor plug elements (R=100Ω, R=33Ω, R=10Ω)
- 1 AV-Module

## Execution

- 1. Set up the experiment according to the circuit diagram.
- 2. Measure voltage and current for various resistances:
  - R=100Ω
  - R=33Ω
  - R=10Ω

3. Note your measured data in the table and calculate each the ratio V/I.

#### Measurement

R (Ω)	100	33	10
V (V)			
I (mA)			
V/I (Ω)			

#### Evaluation

1. Deduce a connection between resistance R and ratio V/I. Which lawfulness can be derived?


## 11. Experiments with DC/AC inverter

Experiment 11.1

## 11.1 Working principle of a DC/AC inverter module
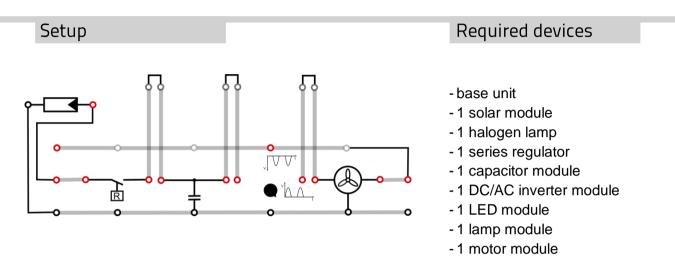
#### Task

Determine the working principle of a DC/AC inverter.



#### Execution

- 1. Set up the experiment as shown in the circuit diagram, initially without the DC/AC inverter. Charge the capacitor completely until the charging control LED of the series regulator turns off.
- 2. Now plug in the DC/AC inverter module and connect the motor module to both outputs of the DC/AC inverter module.
- 3. Adjust the frequency initially to the minimum (0.5Hz). Observe the behaviour of the motor module.
- 4. Now slowly increase the frequency, what do you observe?
- 5. Apply the lamp module and the LED module instead of the motor module. Compare the behaviour of both modules.

#### Evaluation


1. Describe the behaviour of the motor module and name reasons for this!

2. What is the difference between the lamp module and the LED module?

## 11.2 Determination of the output voltage course at the DC/AC inverter
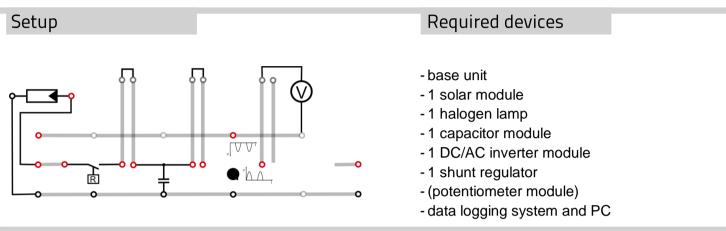
#### Task

Determine the voltage course at the output of the DC/AC inverter module.



## Execution

- 1. Set up the experiment as shown in the circuit diagram, initially without the DC/AC inverter. Charge the capacitor completely until the charging control LED of the shunt-regulator turns off.
- 2. Now plug in the DC/AC inverter module and connect the voltage sensor of the data logging system to both outputs of the DC/AC inverter module.
- 3. Start the data logging and consider the course of voltage. Adjust slowly the frequency of the DC/AC inverter module and observe the course.
- 4. Record the course of voltage respectively for three frequencies for 10 seconds. (Interval: 50 samples per second)

#### Addition:

Connect the potentiometer module in series to a current sensor with both outputs of the DC/AC inverter module. Adjust the  $1k\Omega$ -potentiometer to the minimum and the  $100\Omega$ -potentiometer to the maximum. Record voltage and current with the data logging system.

#### Evaluation

1. Mark the three measurements at different frequencies in a diagram and calculate the frequencies.







#### leXsolar GmbH Strehlener Straße 12-14 01069 Dresden / Germany

 Telefon:
 +49 (0) 351 - 47 96 56 0

 Fax:
 +49 (0) 351 - 47 96 56 - 111

 E-Mail:
 info@lexsolar.de

 Web:
 www.lexsolar.de